

Lastname, Name: _____
ID: _____

Elec-204: Digital Systems Design

Final Exam ¹

June 12, 2010

Duration: 120 min

| Q | Pts | Score |
|-------|-----|-------|
| 1 | 25 | |
| 2 | 10 | |
| 3 | 15 | |
| 4 | 20 | |
| 5 | 10 | |
| 6 | 20 | |
| Total | 100 | |


¹This is a closed-book and closed-notes exam. Please read each question carefully, and give your solution in a formal and clean way. It's the best way to get partial credits. *GOOD LUCK!*

1. [25 pts] Given Boolean function,

$$F(X, Y, Z, W) = \Pi M(3, 4, 11, 12)$$

- (a) Find and list all prime implicants of the F function.
- (b) Find and list all essential prime implicants of the F function.
- (c) Find the minimal two level NAND gate implementation of the F function. Find the gate input cost.
- (d) Find the minimal two level NOR gate implementation of the F function. Find the gate input cost.

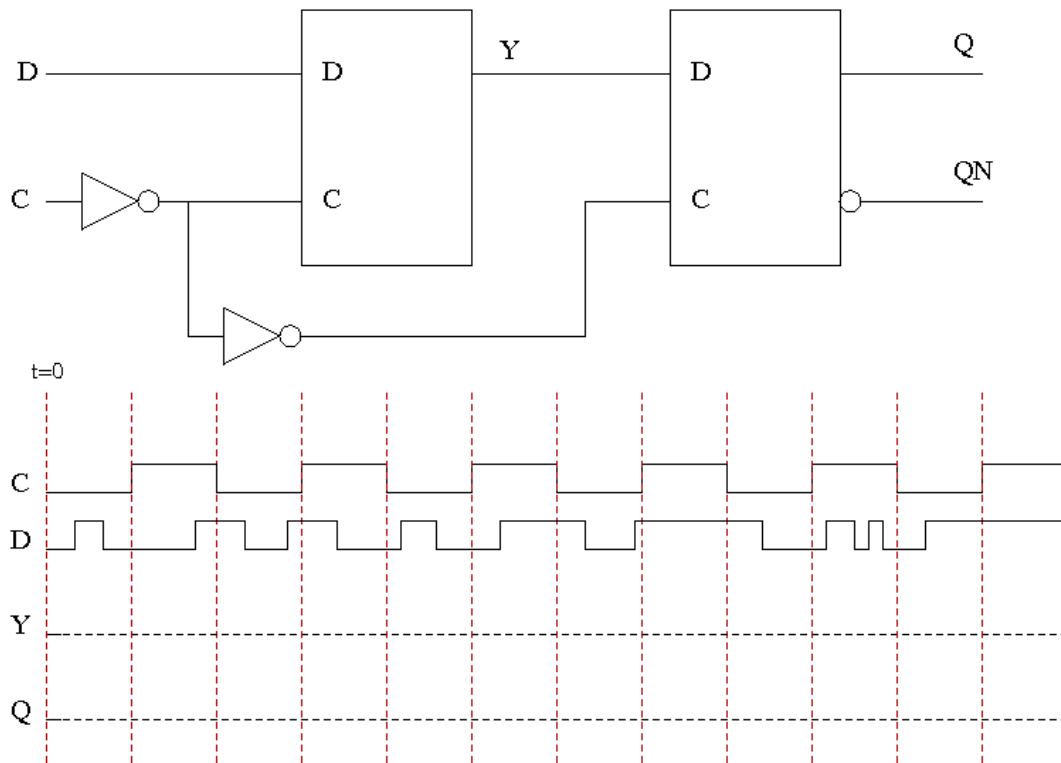2. [10 pts] Perform the timing analysis of the following master-slave flip-flop architecture by plotting the state variables, Y and Q , along with the given clock. You can assume no observable propagation delay in your plots. Note that at time $t = 0$, both Y and Q state variables are at LOW level. (Be careful and plot clean, no partial credits!)



3. [15 pts] A sequential circuit with three D-type flip-flops $Y_1Y_2Y_3$, input X and output Z is defined with the following input/output functions:

$$D_1 = X\bar{Y}_3 + \bar{X}\bar{Y}_1Y_3$$

$$D_2 = \bar{X}(\bar{Y}_3 + Y_2) + X\bar{Y}_2Y_3$$


$$D_3 = X\bar{Y}_3 + \bar{Y}_2Y_3$$

$$Z = Y_3$$

- (a) Find the state table for the circuit and replace the state codes with single letter state identifiers. Note that, states 100 and 111 were unused in the design.


- (b) Check for, identify and combine equivalent states.

 4. [20 pts] A synchronous sequential circuit with input X and output Z is described with the following state transtion diagram.





(b) Design the synchronous sequential circuit using set-dominant master-slave flip flops. A set dominant master-slave flip flop has set (S) and reset (R) inputs. It differs from a conventional master-slave flip flop by setting output state with $S = 1$ and $R = 1$ inputs.

 5. [10 pts] Design a 1024x16 RAM using the following 256x8 RAM blocks and necessary combinational circuit. Note that, 256x8 RAM block has 8 bit data (DATA), 8 bit address (ADRS), chip select (CS), read/write (R/\bar{W}) inputs and a three-state output bus.



6. [20 pts] In the following ASM chart, S is an input signal and R is a 4-bit shift register. The shift left and shift right instructions take zero from the serial inputs. Considering this ASM chart answer the following questions,

 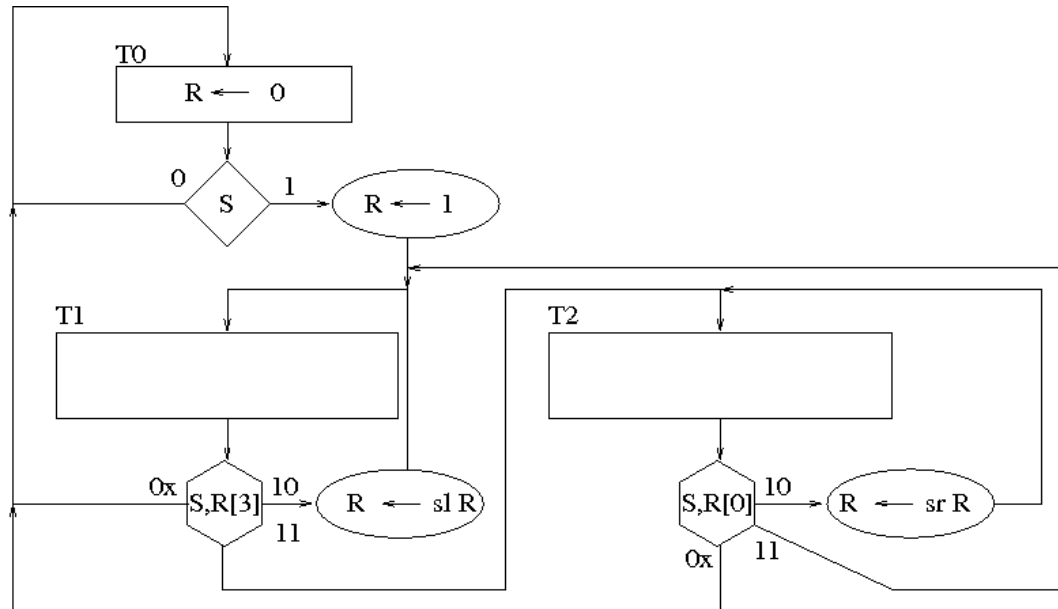- (a) Given the system's clock and S input in the following figure, plot the content of register R and write the present state for each clock cycle **on the figure**. Note that, at the first clock cycle R was reset to all logic zeros. (Be careful and plot clean, no partial credits!)



- (b) Design the control unit of this ASM chart with minimum number of (any type) flip-flops and combinational circuit elements.